

Digital VLSI - EECS4612

Project 2: Post-Layout simulation of a Complex Logic Gate

Instructor: Dr. Amir M. Sodagar

TA: Mohsen Namavar

Winter 2025

Project Description

1. *Schematic Design:*

- Design the schematic for $F = \overline{C} + A \cdot B$ using Cadence Virtuoso.
- Use the following transistor sizing:
 - $L = L_{\min}$, $W_p = 200 \text{ nm}$, $W_n = 150 \text{ nm}$.
- Create a **symbol** for the designed schematic.
- **Note:** For the schematic of this logic function, you can refer to your course slides.

2. *Layout Design:*


- Create a compact layout for the circuit in Cadence Virtuoso Layout Editor.
- You are allowed to use **P-Cells**, but employ abutment techniques (merging shared diffusion regions between transistors) to optimize the area.
- Only **Poly** and **Metal 1** interconnects are allowed. No other metal layers can be used.
- You must draw a layout similar to what you learned in class, with PMOS transistors placed at the top and NMOS transistors placed at the bottom, following standard CMOS layout conventions.
- Ensure the layout passes both Design Rule Check (**DRC**) and Layout vs. Schematic (**LVS**) validations.

3. *Parasitic Extraction:*

- Extract the layout in two configurations to analyze the effect of parasitics on circuit performance:
 - **Without Parasitic Elements:** Perform a layout extraction that includes only the geometric and connectivity information of the layout, excluding parasitic resistances and capacitances.
 - **With Parasitic Elements:** Perform a full layout extraction that includes parasitic resistances and capacitances, which model the physical effects of interconnects and diffusion regions.

 4. Testbench Design:

- Create a separate schematic for the testbench and name it `yourDesignName_tb`. Instantiate the logic circuit three times (We want to simulate designed gate in 3 different configuration). Place a `vdc` instance from the `analogLib` library and connect the **VDD** pins of all instances to a 1.1V DC supply and the **GND** pins to Ground, respectively. Ensure proper connections to all instances.
- Use the `vsource` instance from the `analogLib` library to apply the input signals *A*, *B*, and *C*. The input signals should be follow:



- Assign appropriate input signals and connect a **50 fF load capacitance** to the output of each instance. Use the **Label** feature (L shortcut in Virtuoso Schematic Editor) to assign clear and meaningful net names to each output, such as:
 - `F_Schematic` for the schematic view instance.
 - `F_Extract` for the extracted view without parasitic elements.
 - `F_RcExtract` for the extracted view with parasitic elements.
- Create a **Config View** (as described in the Layout Extraction Tutorial) for the testbench and set the view of the instances as follows:
 1. **Schematic View.**
 2. **Extracted View Without Parasitic Elements.**
 3. **Extracted View With Parasitic Elements.**

5. Post-Layout Simulation:

- Simulate the transient response for the testbench config view and compare the results for the three instances.
- Measure and report:
 - Rise time (t_{LH}) and fall time (t_{HL}).
 - Maximum propagation delay (t_{max}).
 - Power dissipation (P_{diss}).
 - Peak current (I_{peak}).
- Calculate the **maximum operating frequency** of the circuit.
- **Note:** For the definitions of rise time, fall time, and propagation delay, refer to your course slides.
- Explain how parasitic elements (resistance and capacitance) impact the circuit's performance, particularly the rise time, fall time, propagation delay, and maximum operating frequency.

Deliverables:

- A short report in PDF format that includes:
 - A picture of your schematic.
 - A picture of your layout.
 - DRC and LVS results.
 - Simulation waveforms (input and output signals) for all three configuration views (Schematic, Extracted without parasitics, and Extracted with parasitics).
- Cadence design files.

Submission Guidelines

1. Create a single ZIP archive containing all the required deliverables.
2. Name the ZIP file using the following convention:
P2_FirstName_StudentID.zip (e.g., P2_Donald_1234567.zip).
3. Submit the ZIP file through the eClass portal by the deadline: **February 09, 2025, 23:59 (EST)**.

Important Note: No submissions will be accepted through email.

Grading Criteria (out of 10)

Your project will be evaluated based on the following criteria:

- **Schematic Design:** Correct implementation of the schematic, proper transistor sizing, and creation of the symbol (*2 out of 10*).
- **Layout Design:** Compact layout with proper abutment techniques, adherence to design rules, and successful DRC/LVS compliance (*3 out of 10*).
- **Simulation Accuracy:** Accurate transient simulation results for all three configuration views (Schematic, Extracted without parasitics, Extracted with parasitics) and correct comparison of results (*3 out of 10*).
- **Report Quality:** Thoroughness, clarity, and inclusion of all required items (schematic, layout, DRC/LVS results, simulation waveforms, and parasitic impact analysis) (*2 out of 10*).

Resources

- Lecture notes and slides.
- Lab sessions.
- EDA tool tutorials (there are plenty of videos available on YouTube).
- Design rule manuals for the selected technology.

Important Notes

- **Late Submissions:** The submission deadline is final, and no submissions will be accepted after the deadline.
- **Academic Integrity:** Collaboration in understanding concepts is encouraged; however, each student must independently design and create their own schematics and layouts. Plagiarism will result in a failing grade for the project.
- **Seek Help:** If you need clarification or assistance, feel free to contact the TA or instructor during office hours or via email.